

Elkretsanalys, Kontrollskrivning KS1, 2015-02-04 kl 08–10

Hjälpmedel: Ett A4-ark med godtyckligt innehåll (handskriven, datorutskrift, diagram, m.m.).

Kontrollskrivningen har 3 tal, med totalt 12 poäng. Den omfattar ämnet 'Likström' och motsvarar del A i tentamen. Det högre av betygen från KS1 (den här) och från tentans del A kommer att användas vid betygssättning av tentan. Del A är godkänt vid $\geq 40\%$, men glöm inte att tentan kräver också minst 50% räknat över talen i alla delar.

Om inte annan information anges i ett tal, ska: angivna värden av komponenter (t.ex. R för en motstånd, U för en spänningskälla) antas vara kända storheter; och andra storheter (t.ex. strömmen markerad i en motstånd) antas vara okända storheter; och komponenter antas vara idéala.


Lösningar ska uttryckas i kända kvantiteter, och förenklas. Var tydlig med diagram och definitioner av variabler. Kontrollera svarens rimlighet genom t.ex. dimensionskoll eller alternativ lösningsmetod.

Använd återstående tid för att kolla på svaren!

Examinator: Nathaniel Taylor

1) [4p]

a) [1p] Bestäm strömmen i_4 .

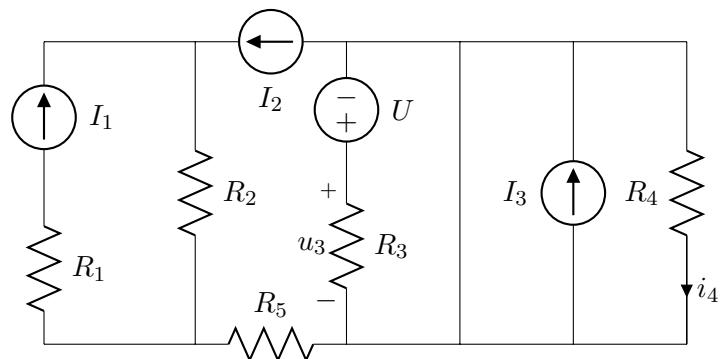

b) [1p] Bestäm spänningen u_3 .


c) [1p] Vilken effekt tar R_2 ?

d) [1p] Vilken effekt levereras av källan U ?

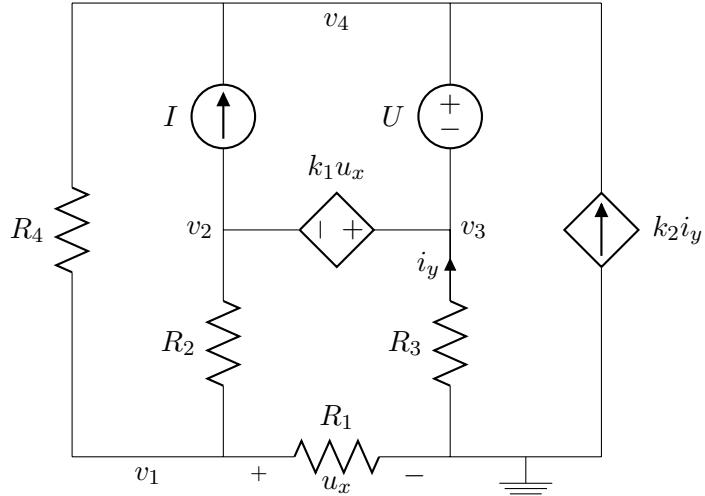2) [4p]

Använd nodanalys för att skriva ekvationer som skulle kunna lösas för att få ut de markerade nodpotentialerna v_1, v_2, v_3, v_4 .


Du behöver bara visa att du kan översätta från kretsen till ekvationerna: du *måste inte* lösa eller förenkla ekvationerna.



3) [4p]

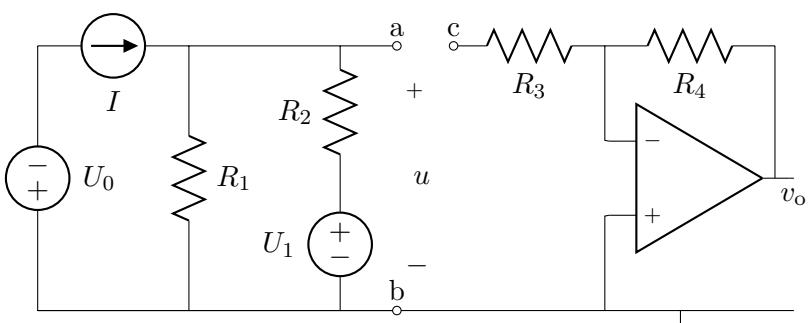a) [3p] Bestäm Theveninekvivalenten sett mellan polerna 'a' och 'b', d.v.s. där spänningen u är markerad.

(Komponenterna R_3, R_4 och opampen försummas, då 'a'-'c' är öppet.)



b) [1p] Polerna 'a' och 'c' kopplas nu ihop (kortslutna). Vad blir potentialen v_o då?

Solutions, EI1120 KS1 2015-02-04

1) Circuit quick-puzzles.

- a) $i_4 = 0$, by Ohm's law, as R_4 is parallel with a short-circuit (0 V)
 - b) $u_3 = U$, by KCL around the loop of R_3 , U and short-circuit: $u_3 + (-U) + 0 = 0$.
 - c) $P_{R_2} = i_{R_2}^2 R_2 = (I_1 + I_2)^2 R_2$, by KCL above R_2 .
 - d) $P_U = U i_U = \frac{U^2}{R_3}$, see answer to part 'b'); one has to be careful about the sign of the current.
-

2)

Extended nodal analysis (“the simple way”)

Let's define the unknown currents in the voltage sources, with the positive direction going into the source's + terminal: call it i_α in source U , and i_β in source $k_1 u_x$.

KCL (outgoing currents) at all nodes except ground:

$$\text{KCL(1)} : 0 = \frac{v_1 - v_4}{R_4} + \frac{v_1 - v_2}{R_2} + \frac{v_1}{R_1} \quad (1)$$

$$\text{KCL(2)} : 0 = \frac{v_2 - v_1}{R_2} + I - i_\beta \quad (2)$$

$$\text{KCL(3)} : 0 = \frac{v_3}{R_3} + i_\beta - i_\alpha \quad (3)$$

$$\text{KCL(4)} : 0 = \frac{v_4 - v_1}{R_4} - I + i_\alpha - k_2 i_y \quad (4)$$

Now there are 8 unknowns ($v_1, v_2, v_3, v_4, i_\alpha, i_\beta, u_x, i_y$), but only 4 equations.

Next, include the further information given by the voltage sources,

$$v_4 - v_3 = U \quad (5)$$

$$v_3 - v_2 = k_1 u_x \quad (6)$$

and also define the controlling variables u_x and i_y in terms of the existing known or unknown quantities,

$$u_x = v_1 - 0 \quad (7)$$

$$i_y = -\frac{v_3}{R_3} \quad (8)$$

There are now 8 equations in 8 unknowns. The systematic way in which this was done is important! There *are* plenty of ways to write a sufficient set of equations, but it is also dangerously easy to write some linearly dependent equations and assume that “ n unknowns, n equations, therefore it's all ok” ... the above method is useful!

Computer-assisted check of solutions to Question 2

We can choose some arbitrary numeric values:

$U = 12 \text{ V}$, $I = 1 \text{ A}$, $k_1 = 0.4$, $k_2 = 3$, $R_1 = 6 \Omega$, $R_2 = 18 \Omega$, $R_3 = 30 \Omega$, $R_4 = 5 \Omega$
and then compare solutions of our equations and a circuit-solver program.

The circuit can be described by the following “netlist” for solving in SPICE. (The extra node 5, and zeroed voltage source Viy , are the way of measuring the current i_y to control CCCS F1.)

```
EI1120_VT15_KS1Q2
V1      4 3   DC   12.0
I1      2 4   DC   1.0
R1      1 0    6.0
R2      2 1    18.0
R3      3 5    30.0
Viy     0 5   DC   0.0
R4      4 1    5.0
E1      3 2   1 0   0.4
F1      0 4   Viy   3.0
.OP
.PRINT DC V(0) V(1) V(2) V(3) V(4)
.END
```

The result from putting the above into SPICE 2g.6 [1983-03-15!] is

```
node potentials:
( 1) 3.1418
( 2) -5.1840
( 3) -3.9273
( 4) 8.0727
( 5) 0.0000
voltage source currents:
v1      4.065E-01
viy     1.309E-01
total power dissipation:
8.38E+00 watts
voltage-controlled voltage sources:
0          e1
v-source  1.257
i-source  5.37E-01
current-controlled current sources:
0          f1
i-source  3.93E-01
```

Putting our equation systems directly into Matlab symbolic toolbox, the ‘extended method’ gives

```
%% solve the equation-system symbolically, for the 6 listed unknowns
% (put an underscore onto variable "I", to avoid it being treated as an imaginary unit
% in matlab symbolic toolbox)
s = solve( ...
'0 = (v1-v4)/R4 + (v1-v2)/R2 + v1/R1', ...
'0 = (v2-v1)/R2 + I_- - ibeta', ...
'0 = v3/R3 + ibeta - ialpha', ...
'0 = (v4-v1)/R4 - I_- + ialpha - k2*iy', ...
'v4 - v3 = U', ...
'v3 - v2 = k1*ux', ...
'ux = v1 - 0', ...
'iy = -v3/R3', ...
'v1, v2, v3, v4, ialpha, ibeta, ux, iy' )

%% if you want, show all the long expressions for the 8 unknowns:
for f=fields(s)', disp(f{1}), simplify(s.(f{1})), end

%% set numeric values for comparison with the SPICE solution
U = 12, I_- = 1, k1 = 0.4, k2 = 3, R1 = 6, R2 = 18, R3 = 30, R4 = 5
% find the result of substituting the above values into the symbolic expressions
for f=fields(s)', fprintf(' %s: %f\n', f{1}, double(subs(s.(f{1})))) ); end
```

```

v1: 3.141818
v2: -5.184000
v3: -3.927273
v4: 8.072727
ialpha: 0.406545
ibeta: 0.537455
iy: 0.130909
ux: 3.141818

```

Fortunately, this matches the earlier solution (after correcting a mistake in the SPICE input file!).

3)

- a) The source U_0 is irrelevant, as it's in series with a current source and we don't want to find any quantities *within* this branch.

Nodal analysis (KCL at a single node) gives, for the open-circuit situation,

$$-I + \frac{u}{R_1} + \frac{u - U_1}{R_2} = 0,$$

whence

$$u_{oc} = U_T = \frac{(U_1 + IR_2) R_1}{R_1 + R_2}.$$

The Thevenin resistance (source resistance) can be found by short-circuit current, or by setting the sources I and U_1 (and U_0 if we haven't noticed that it has no influence) to zero and calculating the equivalent resistance of the circuit. Using the latter approach, we have R_1 and R_2 in parallel, so

$$R_T = \frac{R_1 R_2}{R_1 + R_2}.$$

You really *should* then draw the diagram showing the Thevenin voltage and resistance with the right direction of voltage with respect to the marked terminals!

- b) The usual inverting-amplifier formula can easily be derived for the relation $\frac{v_o}{v_c} = \frac{-R_4}{R_3}$. But we can't just use this together with the open-circuit potential $v_a = U_T$, to find v_o . In this circuit, $v_o \neq \frac{-R_4}{R_3} U_T$. That's because this opamp circuit does not have an infinite input resistance at terminal 'c', and the earlier circuit (left) does not have a zero output resistance at point 'a'.

If a potential v is put on terminal 'c', then a current $\frac{v}{R_3}$ will flow from 'c' to the virtual earth node of the opamp's inverting input, as the non-inverting input is connected to the earth node (current into the virtual earth node leaves it through R_4 ... the opamp's input terminal has no current). And, if a current is drawn from terminal 'a', the voltage u will change compared to its open-circuit value. So when the terminals 'a'-‘c’ are connected (shorted together) a current will flow between them, and the voltage u will depend on the Thevenin voltage and resistance of the circuit on the left *and* on the input resistance of the opamp circuit on the right.

With 'a'-‘c’ connected, we find (by using the Thevenin equivalent and voltage division between R_T and R_3) that

$$u_{ab} = a_{cb} = v_c = U_T \frac{R_3}{R_T + R_3}.$$

The inverting amplifier gain $\frac{-R_4}{R_3}$ *can* be used if we've correctly worked out what v_c is for the complete circuit:

$$v_o = U_T \cdot \frac{-R_4}{R_3} \cdot \frac{R_3}{R_T + R_3} = -\frac{(U_1 + IR_2) R_1}{R_1 + R_2} \cdot \frac{R_4}{R_3} \cdot \frac{R_3}{\frac{R_1 R_2}{R_1 + R_2} + R_3} = -\frac{(U_1 + IR_2) R_1 R_4}{R_1 R_2 + R_1 R_3 + R_2 R_3}.$$